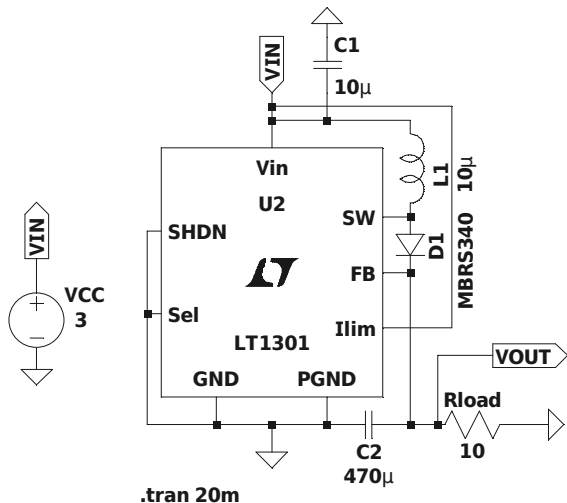


Author: Alexandre DesAulniers
Voltage Boost Converter (Non-Sync - LT1301)



Started with 100u smoothing Capacitor - visible ripple in graph.
Tried 220u & 470u.
470u seems to be the winner, with a charge time of about ~10ms.
Small ripple

Inductor L1 peaks at 1.088A
Triangle still have sharp peaks - we aren't facing inductor saturation

VIN_avg = 2.8579 Watts
VOUT_avg = 2.1496 Watts
We're running at about 75.2% efficiency with 1N5817 Schottky Diode (Vf = 0.5)
77.5% with the PMEG4010BEA
80.30% with the MBR30 - OnSemi